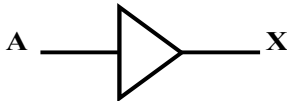
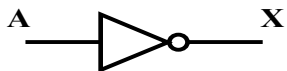
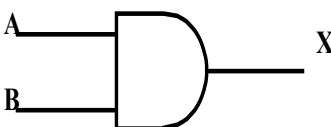
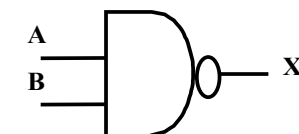
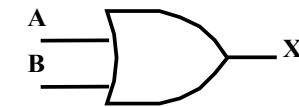
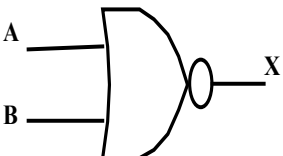

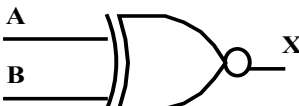



Digital Electronics

See Boolean Algebra for a description of the category as well as references.

NAME	GRAPHICAL SYMBOL	ALGEBRAIC EQN	TRUTH TABLE															
BUFFER		$X = A$	<table><tr><td>A</td><td>X</td></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	A	X	0	0	1	1									
A	X																	
0	0																	
1	1																	
NOT		$X = \overline{A}$	<table><tr><td>A</td><td>X</td></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	A	X	0	1	1	0									
A	X																	
0	1																	
1	0																	
AND		$X = AB \text{ or } A*B$	<table><tr><td>A</td><td>B</td><td>X</td></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	X	0	0	0	0	1	0	1	0	0	1	1	1
A	B	X																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
NAND		$X = \overline{AB} \text{ or } \overline{A*B}$	<table><tr><td>A</td><td>B</td><td>X</td></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	1	0	1	1	1	0	1	1	1	0
A	B	X																
0	0	1																
0	1	1																
1	0	1																
1	1	0																
OR		$X = A+B$	<table><tr><td>A</td><td>B</td><td>X</td></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	X	0	0	0	0	1	1	1	0	1	1	1	1
A	B	X																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
NOR		$X = \overline{A+B}$	<table><tr><td>A</td><td>B</td><td>X</td></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	1	0	1	0	1	0	0	1	1	0
A	B	X																
0	0	1																
0	1	0																
1	0	0																
1	1	0																
EXCLUSIVE-OR (XOR)		$X = A\oplus B$	<table><tr><td>A</td><td>B</td><td>X</td></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	0	0	1	1	1	0	1	1	1	0
A	B	X																
0	0	0																
0	1	1																
1	0	1																
1	1	0																
EQUIVALENCE (XNOR)		$X = \overline{A\oplus B}$	<table><tr><td>A</td><td>B</td><td>X</td></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	X	0	0	1	0	1	0	1	0	0	1	1	1
A	B	X																
0	0	1																
0	1	0																
1	0	0																
1	1	1																

Sample Problems

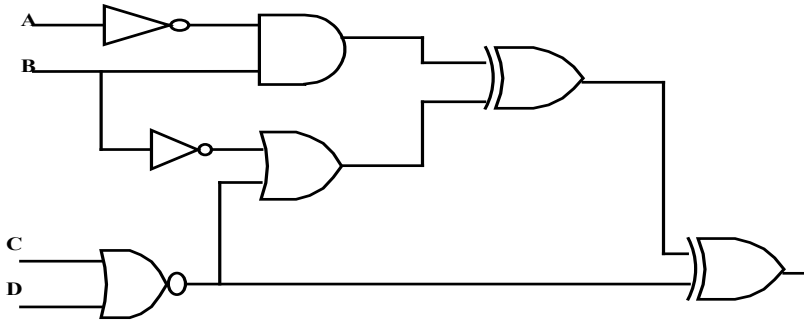Find all ordered 4-tuples (A, B, C, D) , which make the following circuit **FALSE**:



The circuit translates to the following Boolean expression:


$$(\overline{C + D + B}) \oplus (\overline{A}B) \oplus (\overline{C + D})$$

The following table has the following headings: H1 is $\overline{(C + D)}$, H2 is $H1 + \overline{B}$, H3 is $\overline{A}B$, H4 is $H2 \oplus H3$ and H5 is $H4 \oplus H1$, the final expression.

A	B	C	D	H1	H2	H3	H4	H5
0	0	0	0	1	1	0	1	0
0	0	0	1	0	1	0	1	1
0	0	1	0	0	1	0	1	1
0	0	1	1	0	1	0	1	1
0	1	0	0	1	1	1	0	1
0	1	0	1	0	0	1	1	1
0	1	1	0	0	0	1	1	1
0	1	1	1	0	0	1	1	1
1	0	0	0	1	1	0	1	0
1	0	0	1	0	1	0	1	1
1	0	1	0	0	1	0	1	1
1	0	1	1	0	1	0	1	1
1	1	0	0	1	1	0	1	0
1	1	0	1	0	0	0	0	0
1	1	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0

Thus, the 4-tuples $(0,0,0,0)$, $(1,0,0,0)$, $(1,1,0,0)$, $(1,1,0,1)$, $(1,1,1,0)$, and $(1,1,1,1)$ all make the circuit **FALSE**.

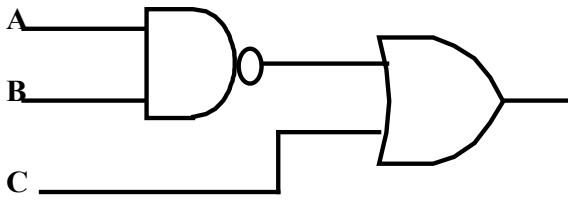Find all ordered triplets (A, B, C) which make the following circuit **FALSE**:



The circuit translates to the following Boolean expression: $\overline{AB} + C$. To find when this is **FALSE** we can equivalently find when the $\overline{\overline{AB} + C}$ is **TRUE**. We can simplify this by applying DeMorgan's Law and cancelling the double *not* over AB to yield ABC . This is **TRUE** when all three terms are **TRUE**, which happens for $(1, 1, 0)$.